

MID TERM PRACTICAL

Computer Organisation

Name: AJIT PAL SINGH RAWAT

Course - MCA, I semester


Father's Name: Mr. AJAYPAL SINGH RAWAT Subject - Computer Organisation

University Roll no.: 2101012

Enrollment no. → PV-21010012

Q.1. NAND Gate: The NAND gate is 'AND' gate succeeded by NOT Gate.
→ NAND gate is an inverted AND gate. (Not + AND)

Symbol:

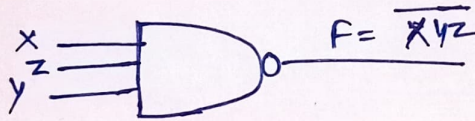

Truth Table:

X	Y	Z	$F = \overline{XYZ}$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$F = \overline{XYZ}$$

Ajit

→ The NAND gate is a combination of an AND gate and NOT gate. They are connected in cascade form.


It is also called Negated And gate.

→ The NAND gate provides the false or low output only when their outputs is high or true.

→ The NAND gate is essential because different types of a boolean function are implemented by using it.

→ The NAND gate has the property of functional completeness. Functional completeness means any type of gate can be implemented by using the NAND gate.

→ NAND . gate diagram

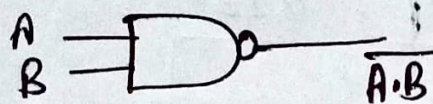

Truth table :

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0