

Name \rightarrow Shivansh Joshi

Sem \rightarrow 1st

University RNO \rightarrow 2101205

Sec \rightarrow A

Exam Type \rightarrow mid sem


Class RNO \rightarrow 56

Ans 1 \rightarrow NAND Gate

A NAND gate ("not AND gate") is a logic gate that produces a low output (0) only if all its inputs are true, and high output (1) otherwise. Hence the NAND gate is the inverse of an AND gate, and its circuit is produced by connecting an AND gate to a NOT gate.


The NAND gate performs the logical NAND operation. NAND gates are known as "Universal gate", which means they are a type of logic gate which can implement any Boolean function without the need to use any other gate type.

Symbol \rightarrow

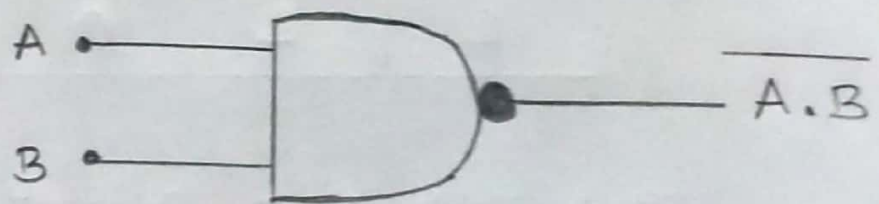

NAND Gate

Circuit Diagram → (IC Diagram)

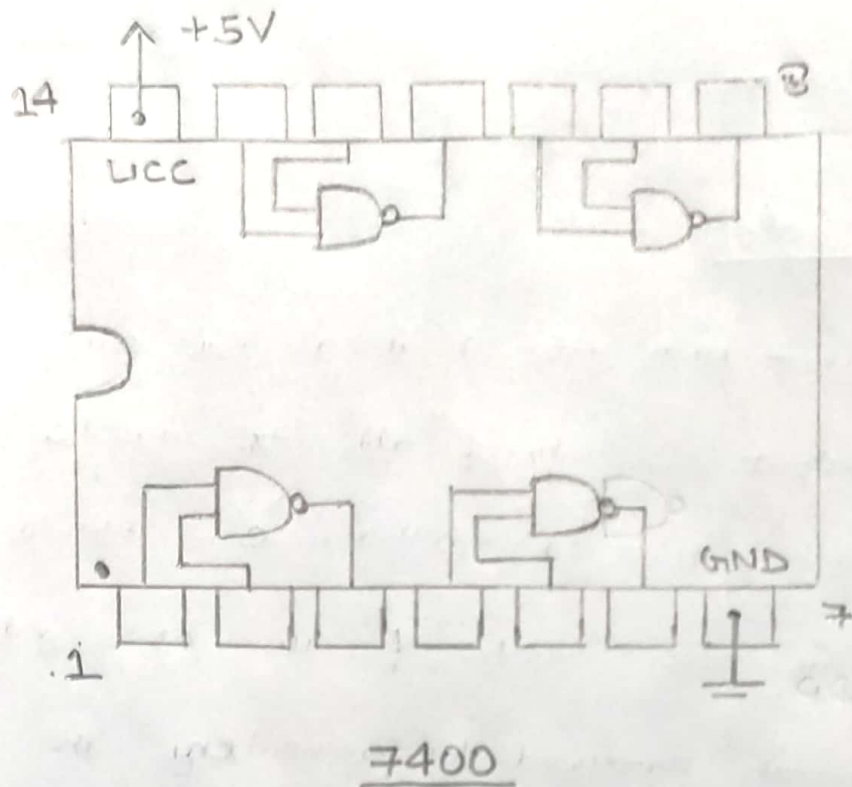

Truth Table →

Input		Output
A	B	$X = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate.