

NAME: Rakshit Thapliyal

Date: 22/03/22

Roll no: 19

Student id: 21711107


Subject: Computer  
Organization

Sec: B

Course: MCA (I<sup>st</sup> sem)

(Ques 2). The NOR Gate is a digital gate that implements Logical NOR- it behaves according to the truth table to the right. A HIGH output (1) results if both the inputs to the GATE are low (0); if one or both input is HIGH (1), a LOW Output (0) results.

(Truth table) :-

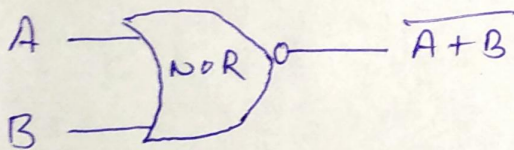

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0



(Circuit diagram) :

