

Name :- Manbir Singh

Father's Name :- Sohan Singh Rawat

Class :- MCA 1st sem Section :- D

Roll No. :- 51

University Roll No. :- 2101257

Student ID :- 21711280

2. NAND gate

In digital electronics, a NAND gate also known as Not-AND which produces a false output only if its both the ~~ex~~ inputs are true.

In NAND gate ~~p~~ takes two inputs '0' or '1' and produces a single output.

It produces an output '0' only if ~~all~~ both the inputs are '1' else the output is '1'.

It can be said that NAND gate produces ~~an~~ a complement output of AND gate.


Function for NAND gate :-

$$F(A, B) = \overline{AB}$$

By De Morgan's law we can say that

$$F(A, B) = \overline{AB} = \bar{A} + \bar{B}$$

Circuit Diagram of NAND gate:-

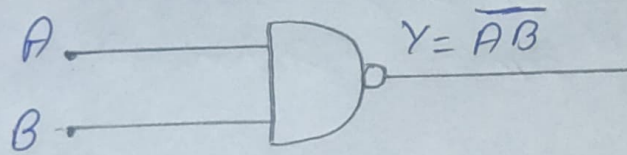

Truth table of NAND gate

INPUTS		OUTPUT
A	B	$Y = \overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

NAND gate on IC 7400

